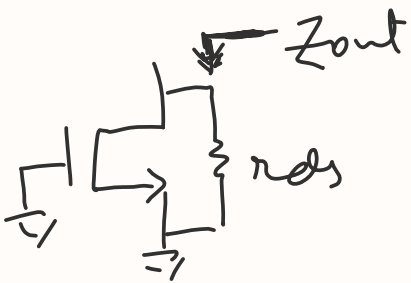


# High Swing Cascode Current Mirror

## ⇒ Introduction:


- High swing cascode current mirror is used instead of usual topology because the output impedance of cascoded current mirror is much higher than usual current mirror.
- Ideally the output impedance of a current source should be "infinite".
- Small signal model for usual and cascoded current mirrors

→



[Usual topology]


$$\rightarrow Z_{out} = r_{ds}$$

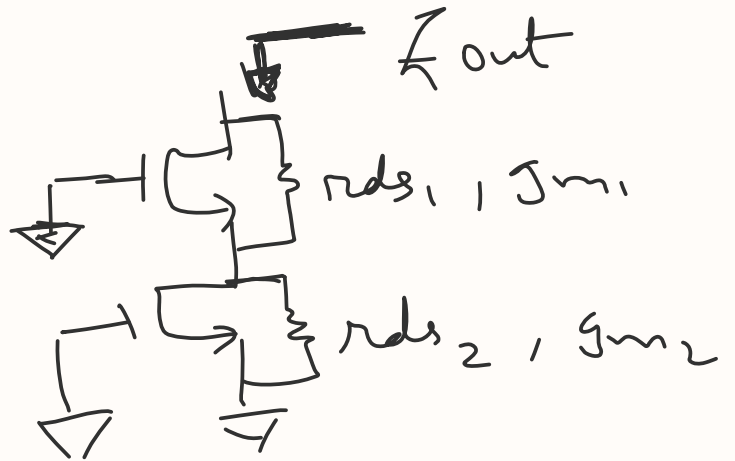

[Cascoded topology]

$$Z_{out} = (g_{m1} r_{ds2} + 1) r_{ds1} + r_{ds2}$$


## → Schematic

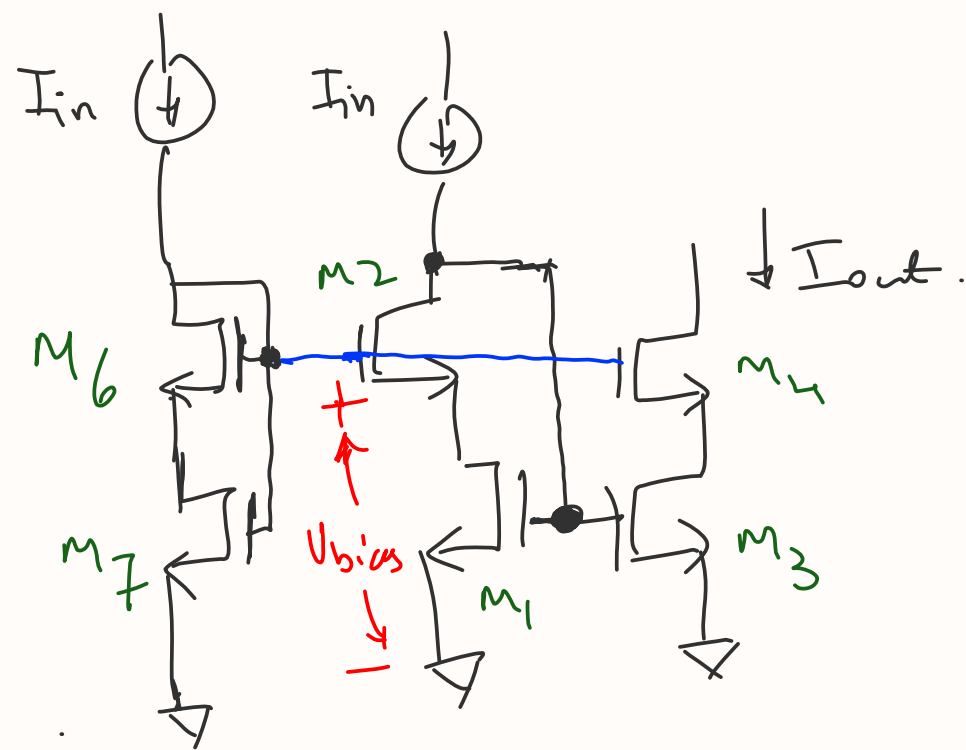

→ The heart of the current mirror is formed by  $M_1$  &  $M_3$ . The  $M_4$  is cascode device  $M_4$  will increase the output impedance.  $M_2$  will ensure that  $V_{DS}$  of  $M_1$  and  $M_3$  is same so that mirroring is accurate.

→ About the bias net,  $M_6$  will be in saturation and  $M_7$  will be in linear region.

## ⇒ Schematic of Cadence

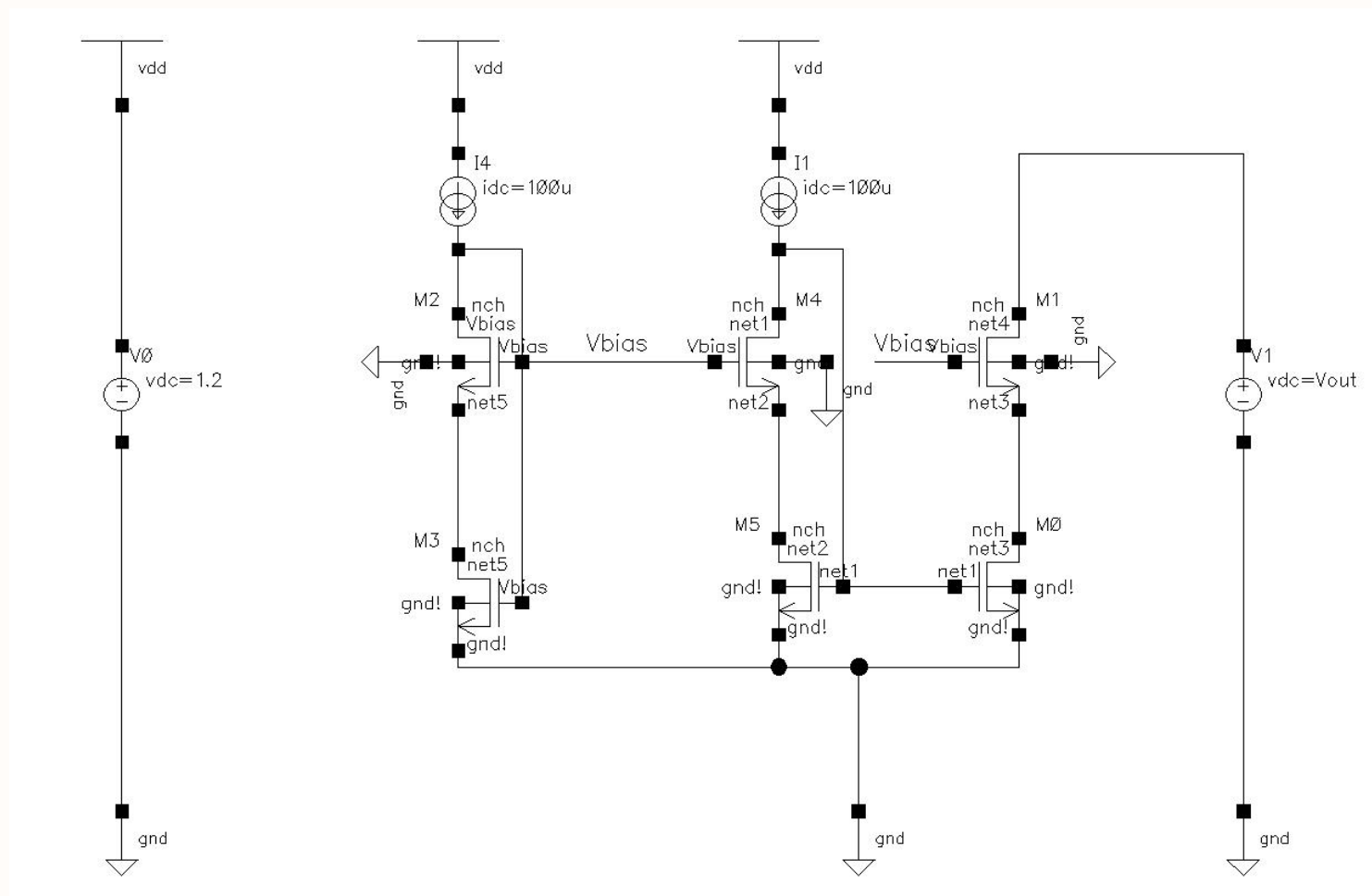

## (2) Design of Cascode Current mirror:

→ We will design current mirror for  $I_{in} = 100\mu A$ .

→ Let's take channel length of all transistors to be  $500nm$ , so that we can avoid the channel length modulation effect majorly. Also take size of  $M_1, M_2, M_3, M_4$  and  $M_6$  equal.

→ We have chosen a  $\left(\frac{g_m}{I_d}\right)_{1,3} = 20 \left(\frac{S}{A}\right)$ , for this value of  $\left(\frac{g_m}{I_d}\right)$  we found  $V_{DSat} = 72mV$ . But the output resistance

of MOSFET changes rapidly around  $V_{DSat}$  so we will keep a little margin of say  $50mV$ . Thus our  $V_{DS3} = \underbrace{72mV}_{V_{DSat}} + \underbrace{50mV}_{\text{Margin.}}$


$$\therefore V_{DS3} = 122mV.$$

→ For  $\left(\frac{g_m}{I_d}\right) = 20$  we found  $V_{GS_{2,4}} = 332.8203mV$  from

$\left(\frac{g_m}{I_d}\right)_{V_{GS}}$  graph. But the graph we plotted does

not consider body effect, so due to body effect the actual  $V_{GS_{2,4}}$  will be a little bit higher. The exact value of it was

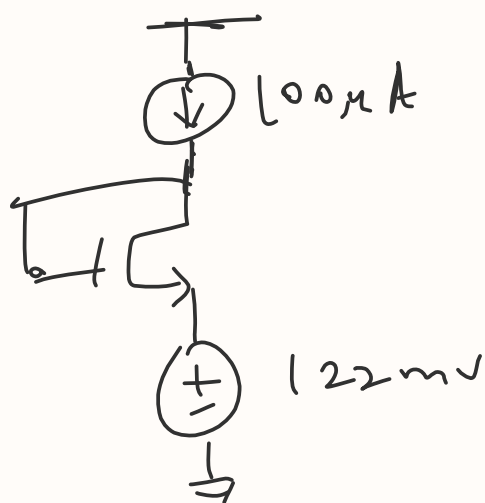found by simulating the circuit in Cadence, the circuit was



→ Note that  $I_{in} = 100\mu A$  is selected

→ From this we found the actual value of  $V_{GS_{2,4}} = 351mV$

→ thus  $V_{bias} = V_{DS1} + V_{GS2}$

$$\therefore V_{bias} = 122mV + 351mV$$

$$\therefore V_{bias} = 473 \text{ mV}$$

→ Now from  $\left(\frac{g_m}{i_d}\right)_{I_{D0}} \stackrel{V_{DS}}{=} \left(\frac{i_d}{\omega}\right)$ , we found  $\omega_1, \omega_2, \omega_3$  &  $\omega_4$ .

$$\rightarrow \omega_1 = \omega_2 = \omega_3 = \omega_4 = 64.943 \text{ } \mu\text{m}.$$


$$\rightarrow \text{Also } M_6 = M_2. \text{ So } L_6 = 500 \text{ nm} \text{ \& } \omega_6 = 64.943 \text{ } \mu\text{m}.$$

→ Now to find  $\omega_7$  :

→ As from the circuit we know  $V_{bias}$  is set by  $V_{GS7}$ , thus from graph of  $V_{GS}$  vs  $\left(\frac{g_m}{i_d}\right)$ , we found that for  $V_{GS} = 473 \text{ mV}$   $\left(\frac{g_m}{i_d}\right) = 10.2767 \left(\frac{\text{S}}{\text{A}}\right)$ . And from  $\left(\frac{g_m}{i_d}\right) \stackrel{V_{DS}}{=} \left(\frac{i_d}{\omega}\right)$ , we can find  $\omega_7$  for  $\left(\frac{g_m}{i_d}\right)_7 = 10.2767 \left(\frac{\text{S}}{\text{A}}\right)$ . The  $\omega_7$  value turns out to be  $\boxed{\omega_7 = 8.771 \text{ } \mu\text{m}}$ .

→ When we simulated the biasing circuit we found that  $V_{GS7} = V_{bias}$  was  $486.5 \text{ mV}$  instead of  $473 \text{ mV}$ .

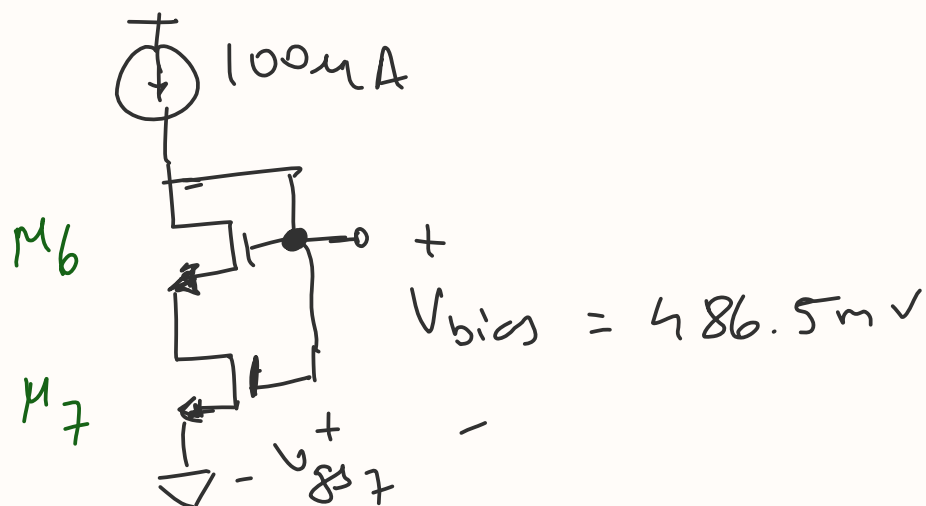→ The biasing circuit made in Cadence is,



$$\begin{aligned} \omega_6 &= 64.93 \text{ } \mu\text{m} \\ L_6 &= 500 \text{ nm} \\ \rightarrow \omega_7 &= 8.771 \text{ } \mu\text{m} \\ L_7 &= 500 \text{ nm} \end{aligned}$$

→ Thus to reduce  $V_{bias}$  we increased the  $w_7$  as by square law model,  $I_D = \frac{\mu_n C_{ox}}{2} \left(\frac{w}{L}\right) (V_{gs} - \underbrace{V_{th}}_{\text{Constant}})^2$ .

$\downarrow$  Constant       $\downarrow$  Constant       $\downarrow$  Constant.

$$\left(\frac{w}{L}\right) \uparrow \Rightarrow V_{gs} \downarrow$$


→ Although square law model is quite inaccurate but it is good enough to get the trends of different quantities for eg: if we increase  $\left(\frac{w}{L}\right) \Rightarrow V_{gs}$  reduces.

→ From simulation it turn out that  $w_7 = 10\mu m$  gives  $V_{gs7} = 475mV$  which is close enough to our required  $V_{bias} = 473mV$ .

→ Thus after getting all the values we will simulate the ckt in cadence to know the swing and accuracy of our current mirror.

→ The setup is as shown below,


$\Rightarrow$

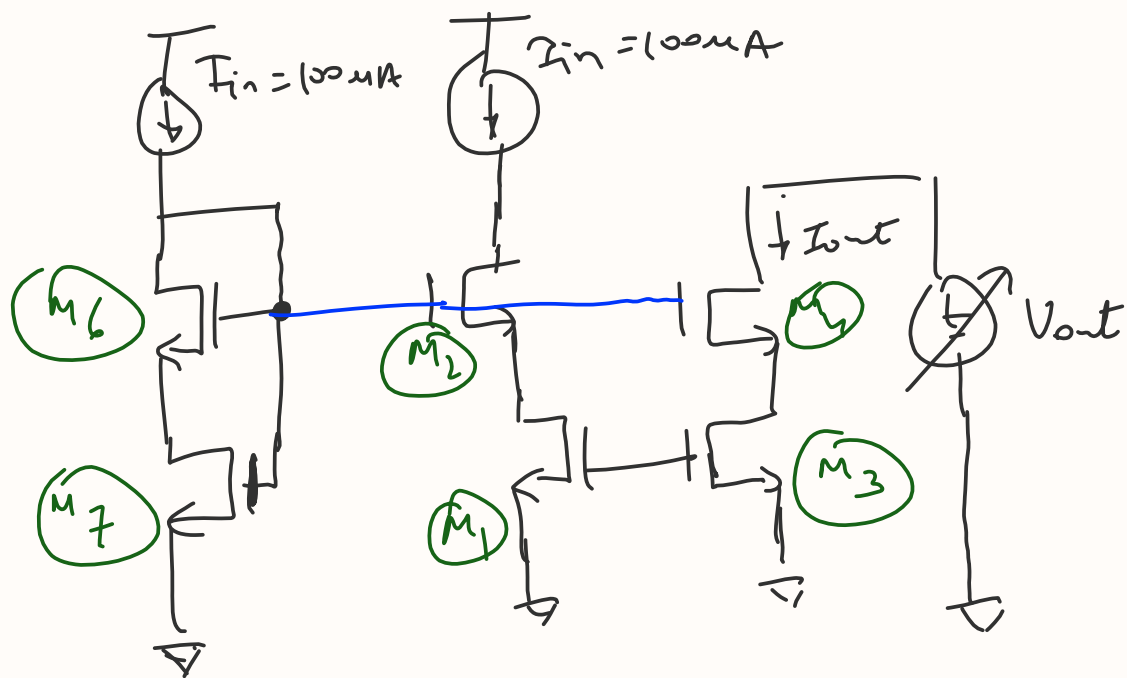




⇒ Simulation result:-

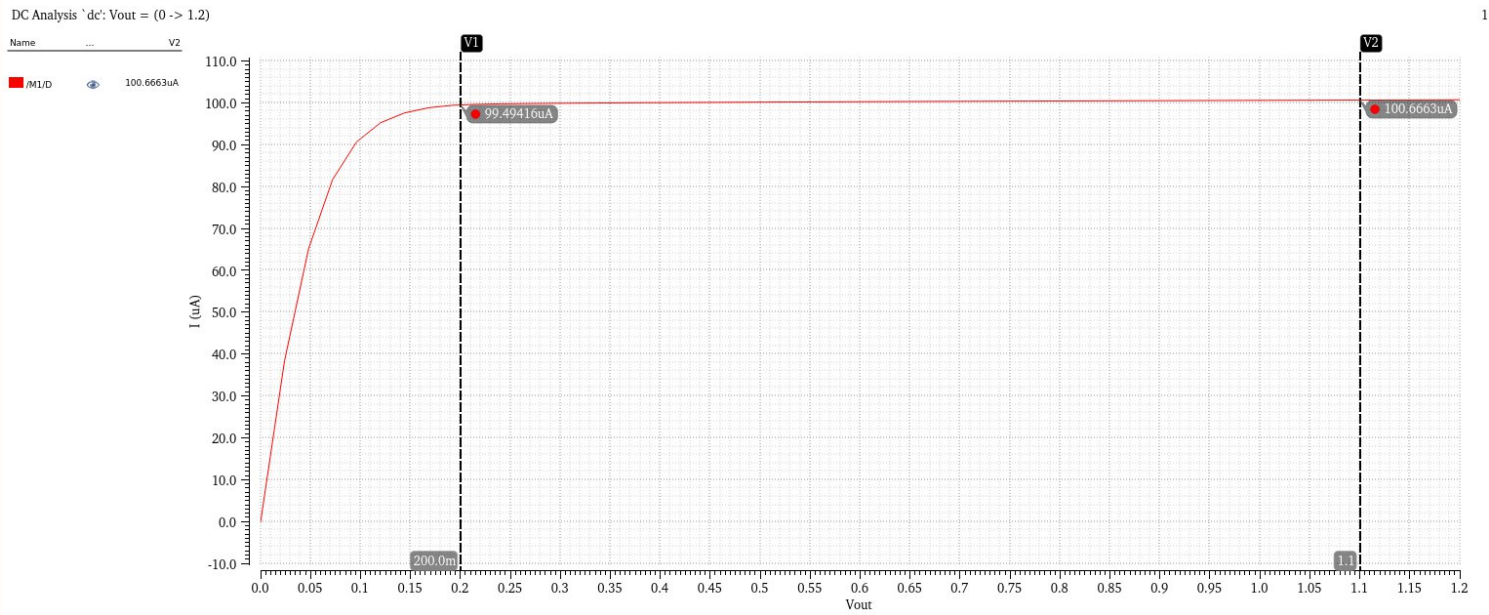Ⓐ  $I_{out} \text{ vs } V_{out}$  :-  $\{V_{out}$  is swept from 0 to  $1.2V$  $\}$   
 $V_{DD}$



Ⓑ % Error curve:-

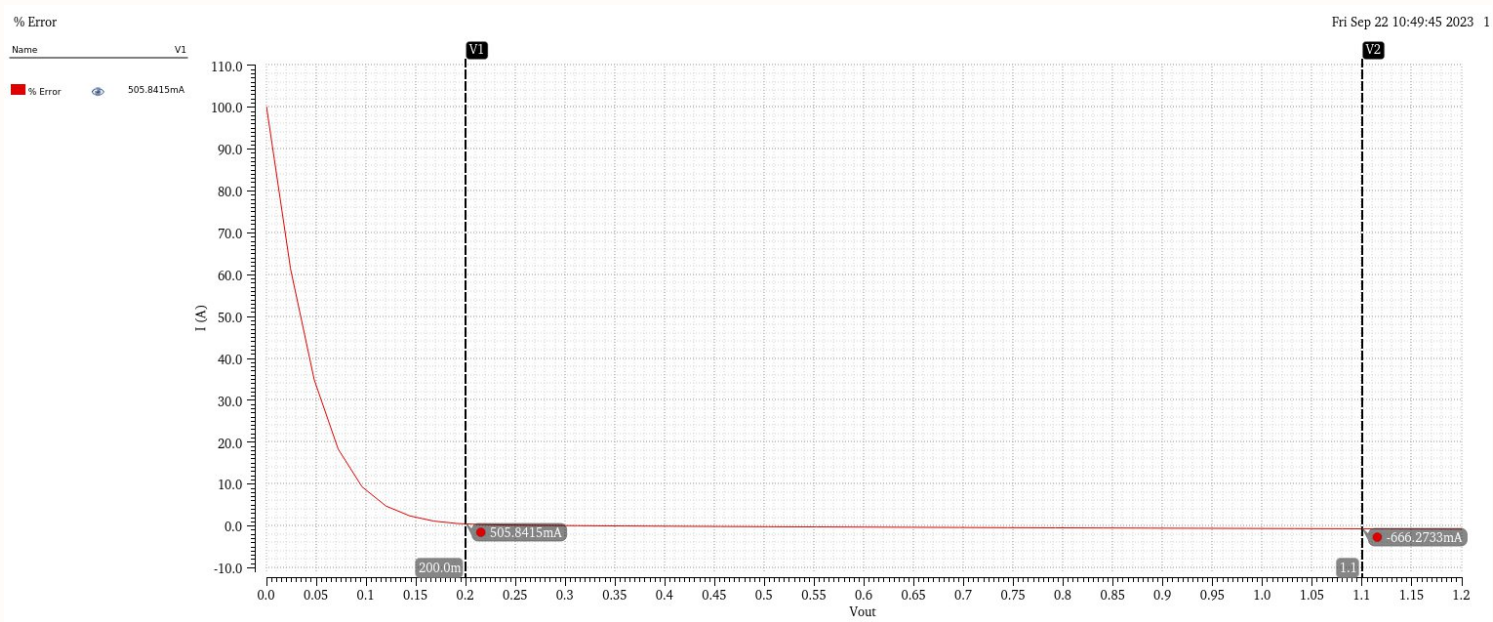→ here we plotted % Error vs  $V_{out}$  curve for  $V_{out}$  being swept from 0 to 1.2V.  
→ % Error is defined as,  $\% \text{ Error} = \frac{100 \mu A - I_{out}}{100 \mu A} \times 100\%$ .



## ⇒ Conclusion:

→ The minimum value of  $v_{out}$  from graph is  $200\text{mV}$  and after that we can see that almost negligible effect of variation of  $v_{out}$  is seen on  $I_{out}$ .

→ Also one important point to note is that minimum  $v_{out}$  is decided on the value of  $V_{bias}$  and  $V_{bias}$

$$V_{bias} = \underbrace{V_{Dsat}}_{\substack{\text{Voltage} \\ \text{of } M_3}} + \underbrace{V_n}_{V_{margin}}.$$

→ And  $V_{Dsat}$  depends on  $\left(\frac{g_m}{i_d}\right)_{1,3}$ .

→ Thus minimum  $v_{out}$  is dependent on  $\left(\frac{g_m}{i_d}\right)$  value we choose and  $V_{margin}$  we choose.